

Lab 13

To Explain the Types and Working of Digital Counters and Implement Binary Counter Using IC

Note: For all the circuits in the tasks, your logic diagrams should be either hand drawn or from the software logicly. Keep them neat and legible. These circuits will be having many connections so, for simulations, make sure that you label the inputs and outputs clearly. Use Label tag in “logically”. You can also edit the pictures of your outputs in “paint” easily.

Tasks

1. Construct a logic circuit for 4-bit Asynchronous Counter using JK Flip Flop. Simulate your circuit to verify the outputs.


4-Bit Asynchronous Counter Using JK Flip Flop

- a) Logic Diagram

Lab-13.

Logic Diagram.

Kashiy Ali
20P-0648.

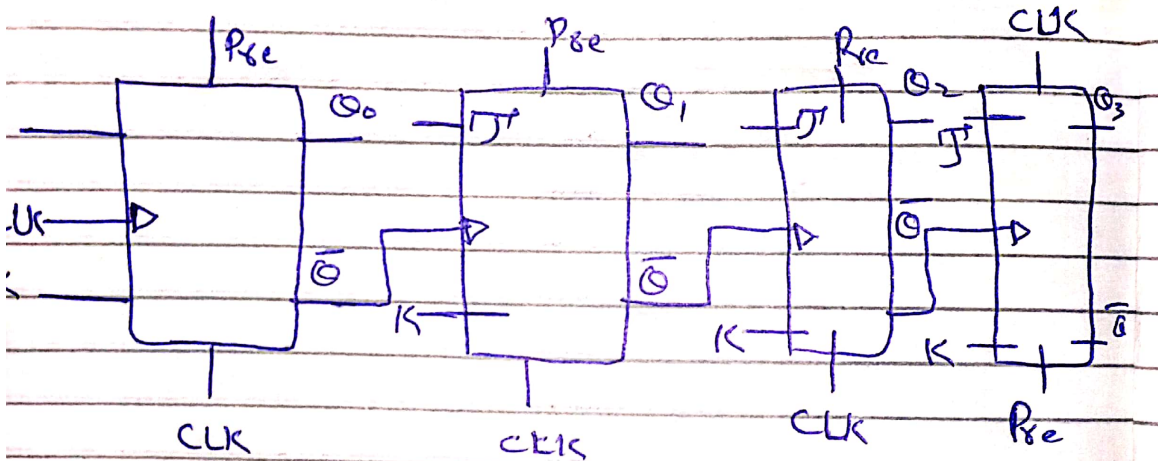

b) Truth Table

The inputs J and K are 1


Clock	Q3	Q2	Q1	Q0
1	0	0	0	0
2	0	0	0	1
3	0	0	1	0
4	0	0	1	1
5	0	1	0	0
6	0	1	0	1
7	0	1	1	0
8	0	1	1	1
9	1	0	0	0
10	1	0	0	1
11	1	0	1	0
12	1	0	1	1
13	1	1	0	0
14	1	1	0	1
15	1	1	1	0
16	1	1	1	1

c) Software Simulation

https://logic.ly/demo/KashifAli/20P-0648/2D2

tech Flex Slate Github kashiiitech | Kashif Ali LinkedIn YouTube Linux_command_line_... Slack | general | NU-P... Slack | COI


Tools Simulate Help

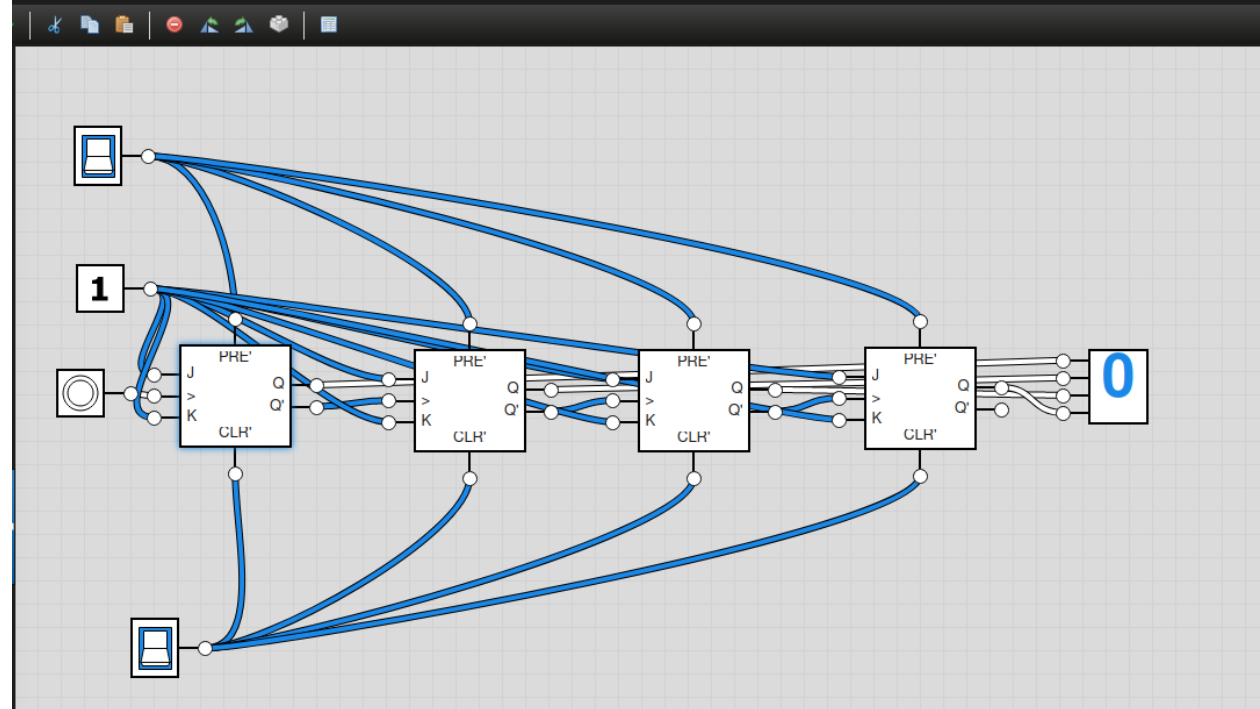

https://logic.ly/demo/KashifAli/20P-0648/2D2


tech Flex Slate Github kashiiitech | Kashif Ali LinkedIn YouTube Linux_command_line_... Slack | general | NU-P... Slack | COLAB


v Tools Simulate Help

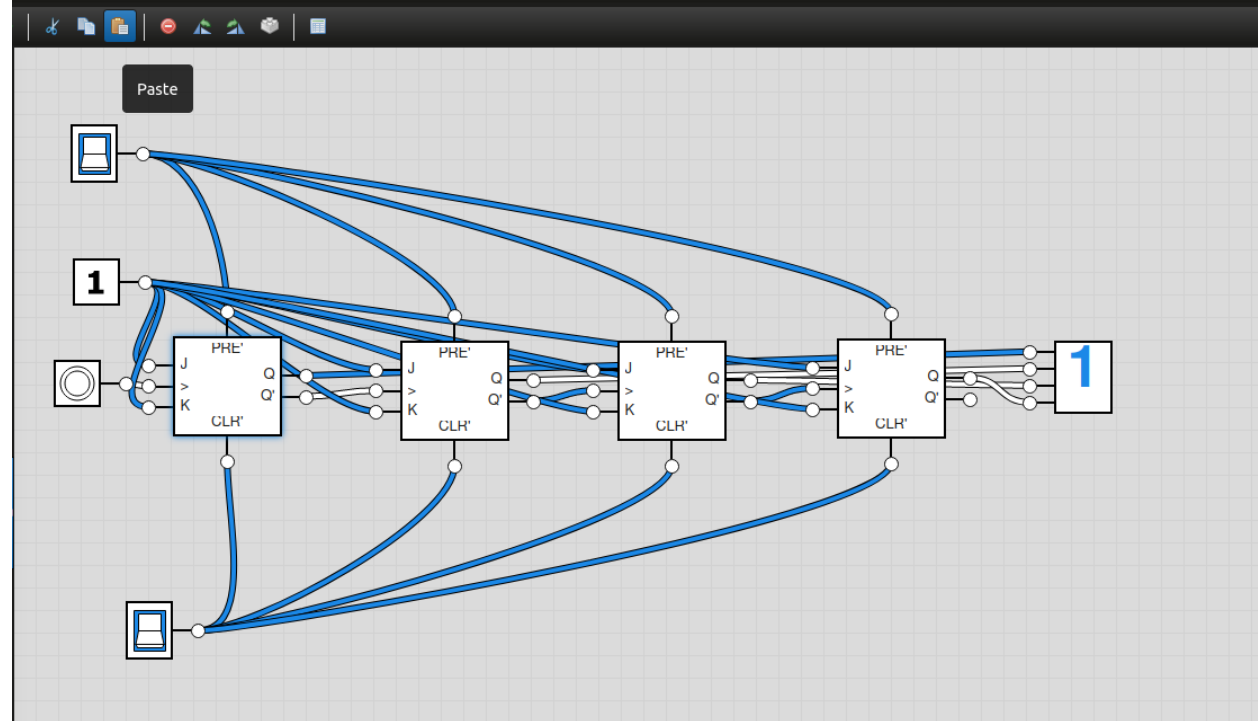


https://logic.ly/demo/KashifAli/20P-0648/2D2

tech Flex Slate Github kashiiitech | Kashif Ali LinkedIn YouTube Linux_command_line_... Slack | general | NU-P... Slack | COI

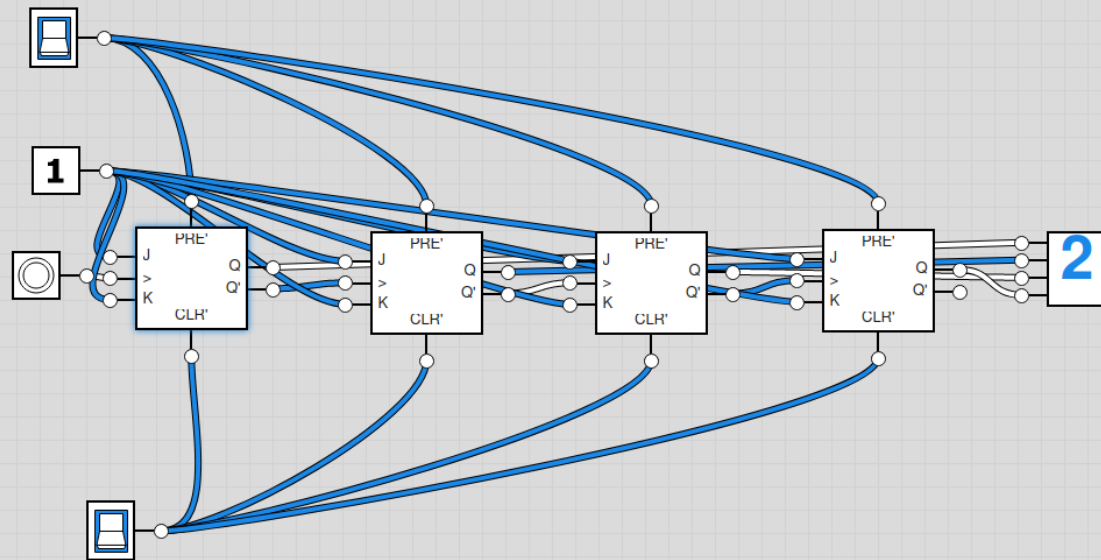

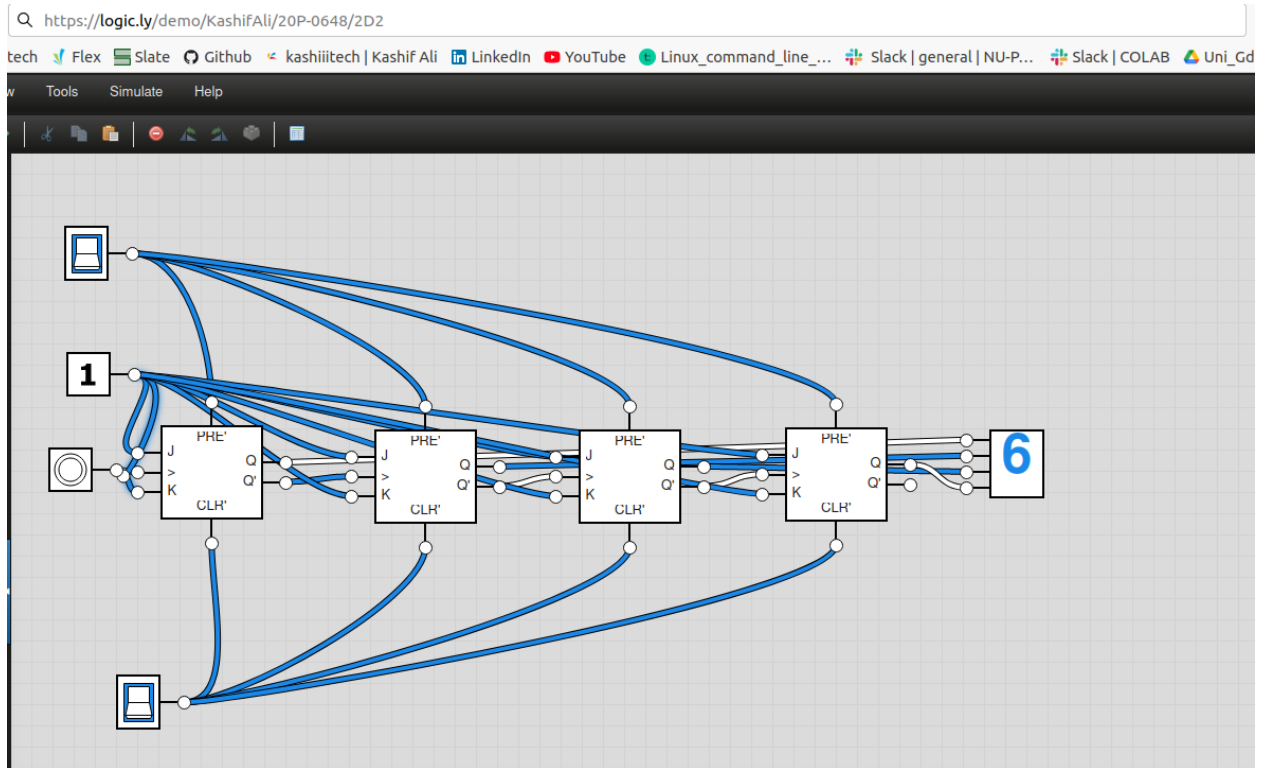

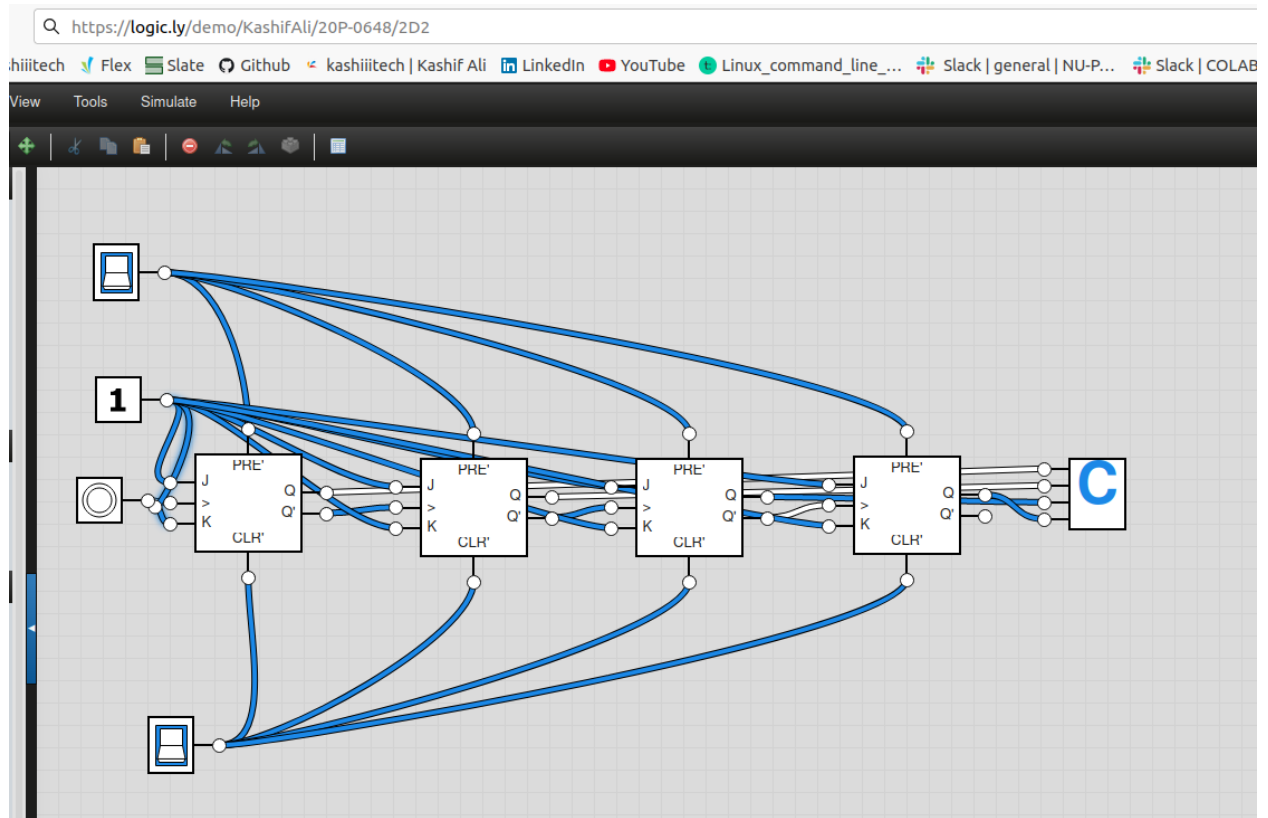


2. Construct a logic circuit for 3-bit Synchronous Counter using JK Flip Flop. Simulate your circuit to verify the outputs.

a) Logic Diagram

Lab-13.

Logic Diagram.

Kashiy Ali
20P-0648.

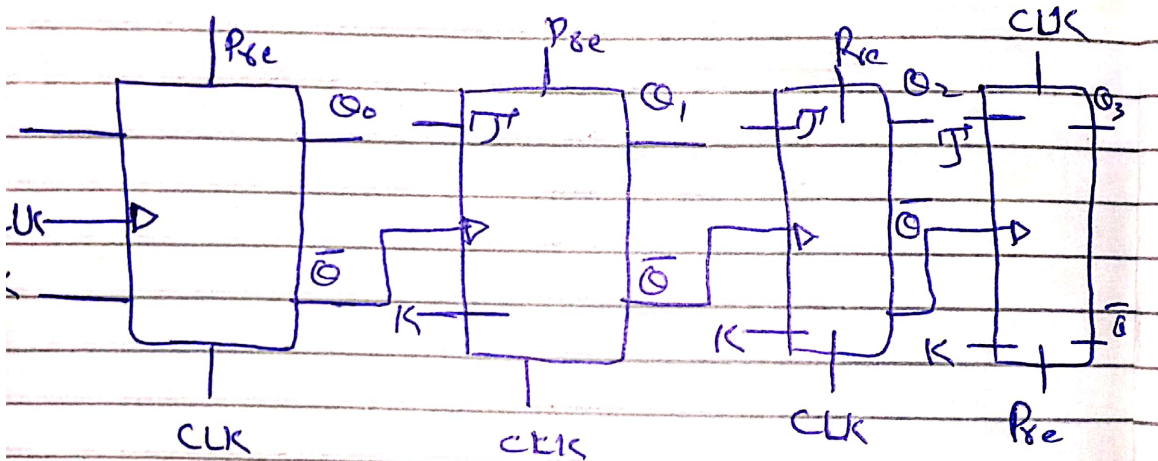

b) Truth Table

J2	k2	J1	K1	J0	K0	Q2	Q1	Q0
1	X	1	X	0	X	0	0	0
1	X	0	X	X	1	0	0	1
0	X	X	0	1	X	0	1	0
0	X	X	1	X	1	0	1	1
X	0	0	X	1	X	1	0	0
X	1	1	X	X	1	1	0	1
X	0	X	0	1	X	1	1	0
X	1	X	1	X	0	1	1	1

c) Software Simulation

https://logic.ly/demo/KashifAli/20P-0648/2D2

ashiitech Flex Slate Github kashiitech | Kashif Ali LinkedIn YouTube Linux_command_line_... Slack | general

View Tools Simulate Help

