

Lab 6

To Demonstrate the Working of Binary Subtractor

Note: You may draw all the logic diagrams with hand and paste the pictures here or on logicly software with your name, roll number & section mentioned in your workspace. Make sure that all of your connections are clearly visible and distinguishable.

Tasks

1. **Construct a logic circuit for half and full subtractor with the help of truth table/Boolean expression. Also write the Boolean expression for output(s).**

Half Subtractor

- a) Truth Table
- b) Boolean Expression (Simplified)
- c) Logic Diagram

Q No 1. Part (a) Truth table.

	A	B	D _{bb}	Borrow
	0	0	0	0
m ₁	0	1	1	0
m ₂	1	0	1	0
	1	1	0	1

Part (b) Expression (Simplified)

$$D = m_1 + m_2$$

$$D = \bar{A}B + A\bar{B}$$

$$D = A \oplus B$$


$$B = m_1$$

$$B = \bar{A}B$$


The Equation of Borrow.

The Equation of Difference

Part (c) Logic diagram

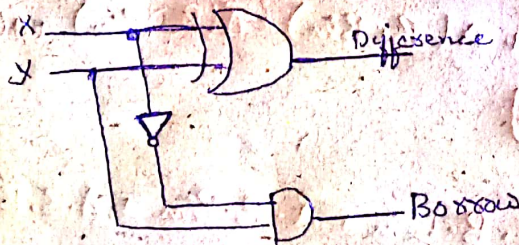

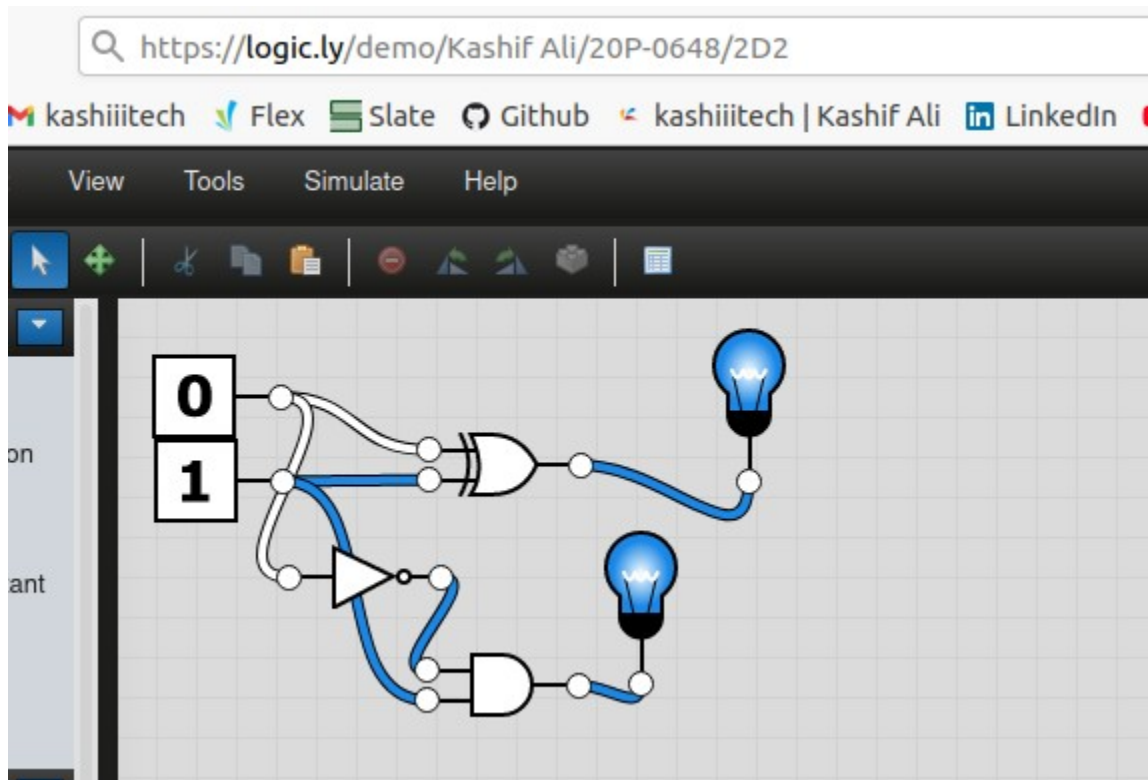- d) Software Simulation ([Show here your results for each combination that gives a high output](https://logic.ly/demo/Kashif%20Ali/20P-0648/2D2))



Full Subtractor

- a) Truth Table
- b) Boolean Expression (Simplified)
- c) Logic Diagram

Full Subtractor

Part (a) Truth table

Inputs			Outputs	
A	B	Bin	D	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Part (b) Expression (Simplified)


$$\begin{aligned}
 \text{Difference} &= \bar{A} \cdot \bar{B} \cdot \text{Bin} + \bar{A} \cdot B \cdot \bar{\text{Bin}} + A \cdot \bar{B} \cdot \bar{\text{Bin}} + A \cdot B \cdot \text{Bin} \\
 &= \bar{A} (\bar{B} \cdot \text{Bin} + B \cdot \bar{\text{Bin}}) + A (\bar{B} \cdot \bar{\text{Bin}} + B \cdot \text{Bin}) \\
 &= \bar{A} (B \oplus \bar{\text{Bin}}) + A (\bar{B} \oplus \text{Bin}) = \bar{A} (B \oplus \text{Bin}) + A (\bar{B} \oplus \text{Bin})
 \end{aligned}$$

$$= A \oplus B \oplus \text{Bin}$$

$$\text{Borrow} = \bar{A} \bar{B} \text{Bin} + \bar{A} \cdot B \cdot \bar{\text{Bin}} + \bar{A} \cdot B \cdot \text{Bin} + A \cdot B \cdot \text{Bin}$$


$$\text{Borrow} = \bar{A} \cdot \bar{B} \cdot \text{Bin} + \bar{A} \cdot B (\bar{\text{Bin}} + \text{Bin}) + A \cdot B \cdot \text{Bin}$$
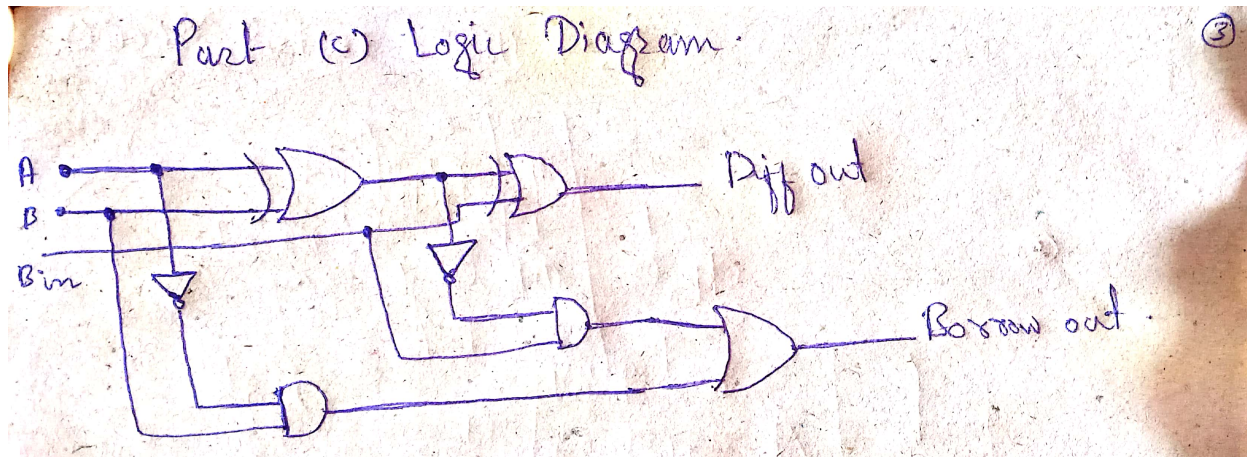
$$= \text{Bin} (\bar{A} \oplus B) + \bar{A} B$$



Scanned with CamScanner

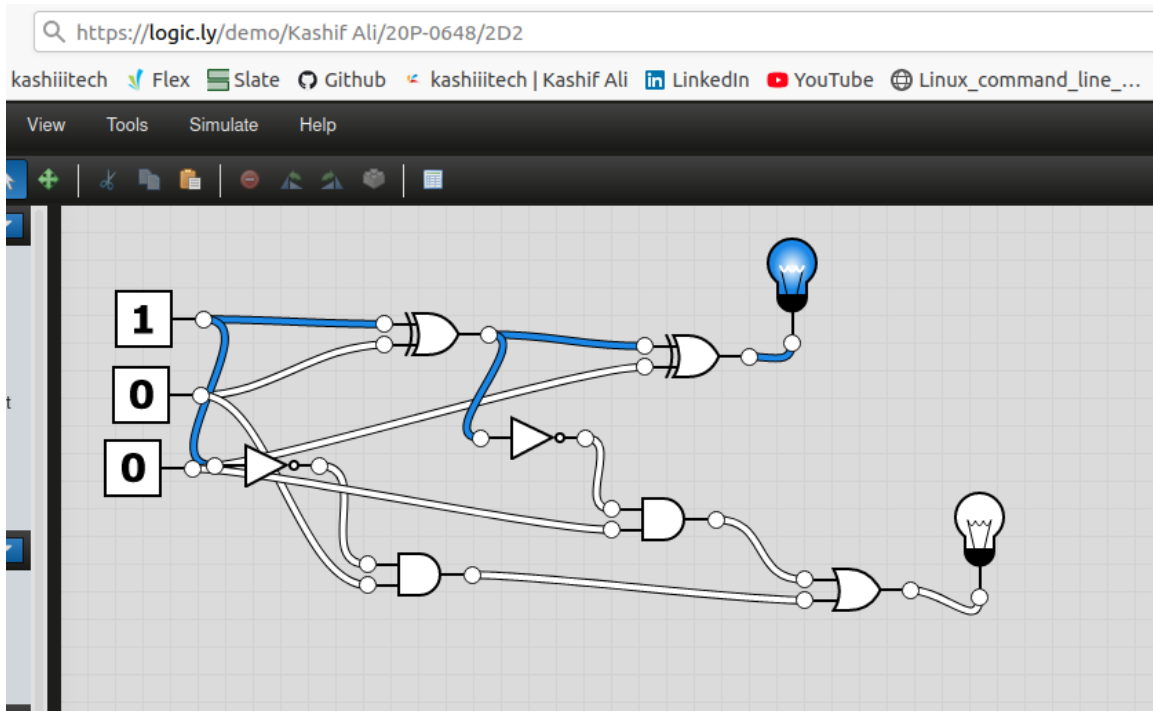- d) Software Simulation (Show here your results for each combination that gives a high output)




2. A full subtractor can be implemented using 2-half subtractors.

Demonstrate the logic diagram for the said circuit. Simulate your circuit for the verification of results.

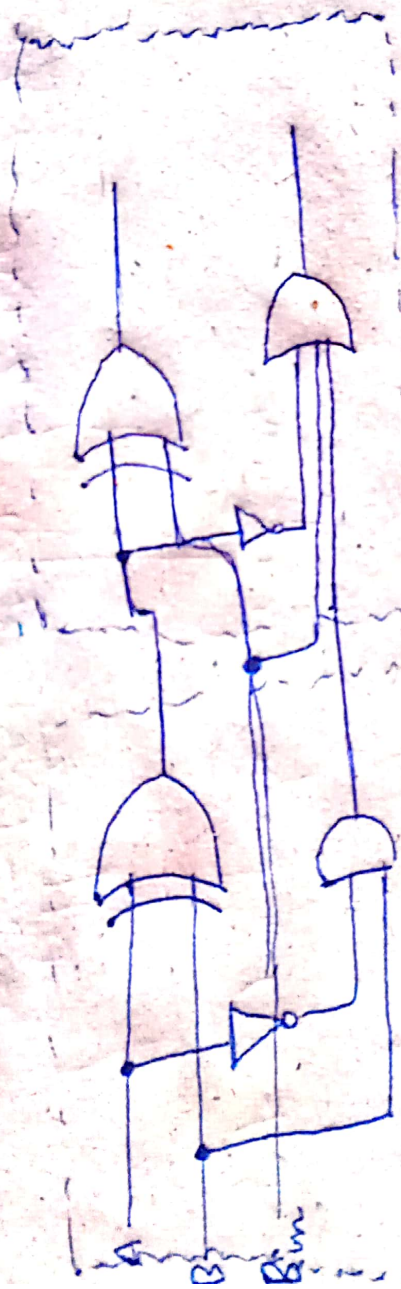a) Logic Diagram of Full Subtractor using 2-Half Subtractor

Q No 2:- Part (a)
Logic diagram of full Subtractor using two half Subtractor



First half Subtractor

Second half Subtractor

b) Software Simulation (Show here your results for each combination that gives a high output)

