

Design a counter(up/down) for first 4 odd numbers(binary).

Requirement:

State Diagram

Next-State Table

Flip-Flop Transition Table

Karnaugh Maps

Logic Expressions for Flip-Flop Inputs

Counter Implementation (Circuit)

Hints: Get Help from figure 9-22 and 9-26...9-28